

Slope Compensation for Grid-tied Battery Boost Converter using Simulink from TI

Note that the slope of the downward inductor current is used (scaled by 0.5 - 0.75) even though the control circuit only sees the rising inductor current. It doesn't matter if the circuit is a buck or boost it is the downward inductor slope we are interested in.

Step 1 Calculate down slope of boost worst case tolerance

$$S(L) = \frac{V_{in(min)} - V_{out}}{L(min)}$$

$$L = 94 \mu H \times 0.8 = 75 \mu H$$

$$V_{in} = 28 \text{ cells} \times 3.2 = 89.6$$

$$V_{out} = 160 \text{ V}$$

$$\frac{89.6 - 160}{75 \mu H} = -0.937 \text{ A}/\mu\text{sec}$$

Step 2 W/A

Step 3 Calculate equivalent down slope Ramp

$$VS(L)' = S(L) \cdot R_{sense}$$

Now I have a difference opamp with gain $\frac{10000}{330} = 30.30$

(Note the problem I see with this step is: the control never sees the down slope through R_{sense} . But let's go with it.)

$$R_{sense} = 0.002 \text{ Ohms} \quad 0.937 \times 0.002 \times 30.30 = 0.05670 \text{ V}/\mu\text{sec}$$

Step 4 Calculate the Oscillator charge slope

$$VS(osc) = \frac{d(V_{osc})}{T_{on}} \quad \text{Now for the UCC2800}$$

$$d(V_{osc}) = 2.45 \text{ V}$$


$$\text{Rise time} = R_T C_T$$

$$\text{Fall time is } 130 \cdot C_T$$

$$R_T = 30 \text{ k} \quad C_T = 200 \text{ pF}$$

$$\text{Rise time} = 6 \mu\text{Sec}$$
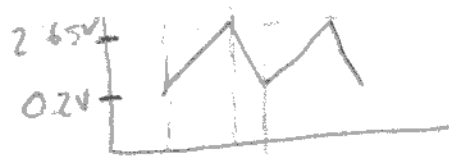
$$\text{Fall time} = 0.026 \mu\text{Sec}$$



$$\therefore VS(ox) = \frac{2.45}{6 \mu\text{Sec}} = 0.408 \bar{3} \text{ V}/\mu\text{Sec}$$

$$\text{or } \frac{1.5}{200 \times 10^{-9} - 30 \text{ k}} = 250 \text{ kHz} = 4 \mu\text{Sec}$$

$$\frac{2.45}{4 \mu\text{Sec}} = 0.6125 \text{ V}/\mu\text{Sec}$$

Step 5 Generate Ramp Equations

$$R_2 = R_1 \cdot \frac{VS(ox)}{VS(L)' \cdot M}$$

$$R_1 = 1 \text{ k} \quad M = 0.75$$

$$\therefore R_2 = \frac{1 \text{ k} \times 0.408 \bar{3}}{0.05670 \times 0.75} = 9.56 \text{ k Ohms}$$

$$\frac{1 \text{ k or } 0.6125}{(0.05670 \times 0.75)} = 14.3 \text{ k Ohms}$$